

GATE

1. What is the boolean expression for the output f of the combinational logic circuit of *NOR* gates given below?

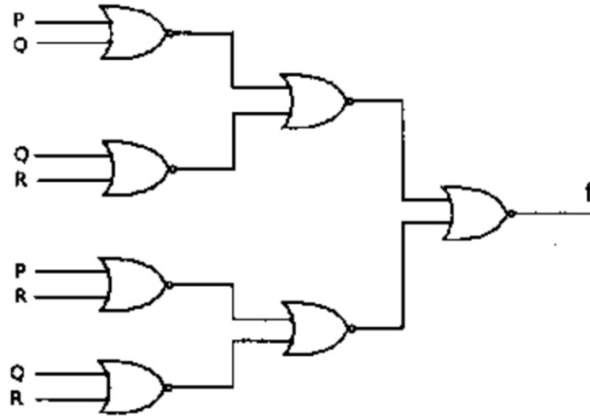


Figure 1:

- (a) $\mathbf{Q + R}$
- (b) $\mathbf{P + Q}$
- (c) $\mathbf{P + R}$
- (d) $\mathbf{P + Q + R}$